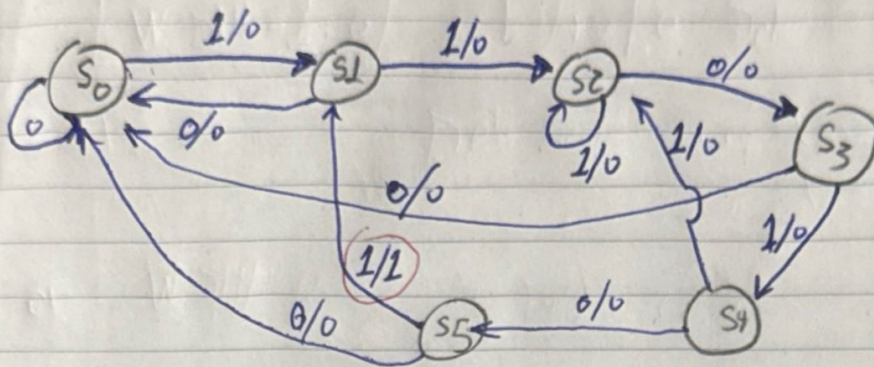



Sequence detector

Mealy overlapping $\rightarrow (110101)$
 110101



ال Nonover هو نفس ال design بس لما اوصل ل S5
 هرجع ل S0 انا كان جه 1, 0

Moore overlapping $\rightarrow (110101)$

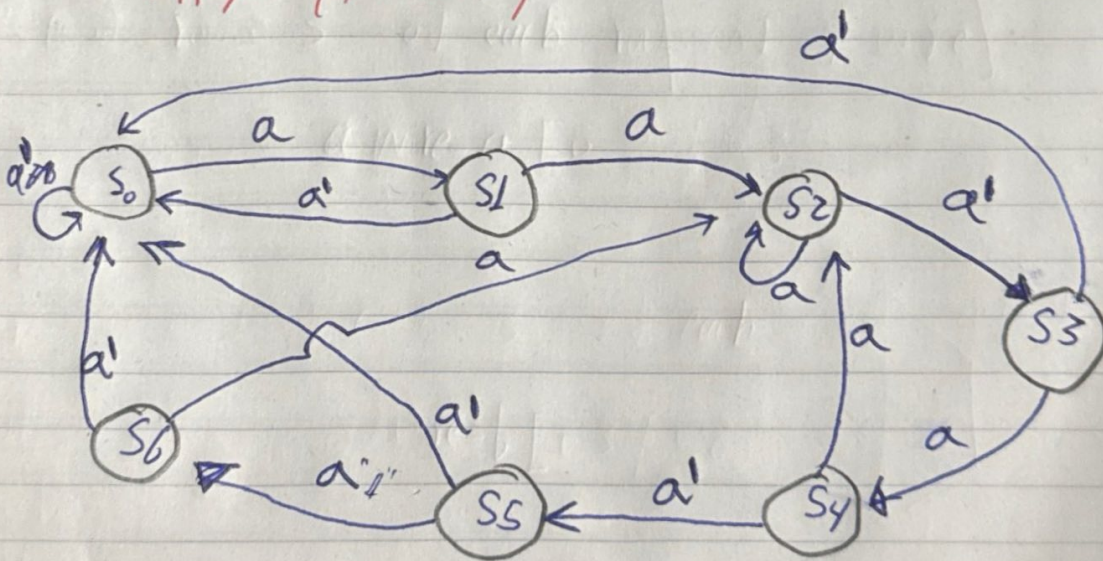

ال Nonover لما يبقا S6 وبعي واحد هرجع ل S1